DENSON ELECTRONICS CORPORATION

Rockville, Connecticut

Instructions Only - 50¢ - Stock No. 779 1698 MONOSCOPE

P.O. Box 85 Longview Street Rockville, Conn.

CONCEPT

VIEWING

NEW

TEST PATTERN MONOSCOPE TUBES FOR CLOSED-CIRCUIT APPLICATIONS

Rockville, Conn. Area Code 203


NEED A STABLE TEST SIGNAL SOURCE FOR ONLY \$9.95

AND A FEW PARTS FROM YOUR JUNK BOX???? Here is the easiest way to get your Camera, Transmitter or Monitor Set up and operating properly. Our Type 1698 Test Monotron tube with a few parts from an old TV set or the usual electronic experimenters clutch pile used in the simple circuit supplied with the tube gets you started in Closed Circuit or Amateur Television Systems. Simpler than a flying spot scanner-LESS fussy than a camera, this pattern generator produces a series of figures and numbers from the self-contained pattern. Stock No. 700FA-2 ONLY Stock No. 700FA-2 ONLY \$9.95 plus postage - Ship. Wt. 3 lbs., #779 Inst. ONLY 500 #710 6"x6" mu-metal for shield \$3.95 #713 14 Pin socket w attached lead \$1.50 711 Model MSN Power Trans. 18.95 716 400 MA 400 PIV Diodes for D1-D-6 45/ea

Have you ever sat at the workbench for hours on end running final checks on a newly constructed piece of ATV gear and found yourself-capacitors are in MFD unless otherwise stated. Component values in direct need of a fixed video test signal? Probably so, and if you'renot shown on the schematic are given in the parts it at the end of a fixed video test signal? Probably so, and if you'renot shown on the schematic are given in the parts it at the end of a fixing spot schematic are given in the parts it at the end of a fixing spot schematic are given in the parts it is at the end of a fixing spot schematic are given in the parts it is at the end of a fixing spot schematic are given in the grade of the fixing spot schematic are given in the grade of the fixing spot schematic are given in the grade of the fixing spot schematic are given in the grade of the first video and is not schematic are given in the spot schemati CONSTRUCTION: Fig. 1 shows a complete schematic of a simple allaways created interest amount ATV ers for purposes of generating will further protect against stray magnetic fields including the earth's field. (3) Use an electrostatic shield over the signal plate is bfixed test patterns, its cost until recently has been prohibitive. portion of the tube to prevent stray RF pickups such as those caused. by nearby AM broadcast stations.

page 1

VIEWING CONCEP

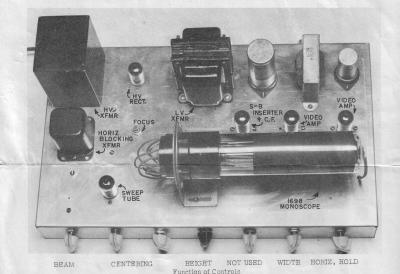

MONOSCOPE CAMERA DENSON ELECTRONICS CORPROCKVILLE, CONNECTICUT

A couple changes which were recently made for improved piz quality. They are: Grounded pin 6 of the monoscope instead of connecting it to point B on the diagram. Results in improved astigmatism with little sacrifice in qain. Changes the .002 waveshaping condenser (this is the one shown connected from the junction point of the LK resistor and the .0016 capacitor in the horizontal osc plate circuit) to a .001. Improved the horizontal pulse by changing to this lower value. Changed the 16k which connects the 4700 ohm resistor from the plate circuitry of the vertical discharge tube to pin 7 of V-3B (syne tube) to 6800 ohms. Improved the vertical sync clipping. A little mu-metal shield is needed to prevent beam distortion.

Additional Components Available from DEC Stock No. Type Socket for Vidicon New High Resolution Vidicon Direct Drive Deflection 59.95 Yoke and Focus Coil Type 5527 Electrostatic Camera Tube New 50.00 1698 - 2 inch Electrostatic Test Monotron SPEC. 9.95 700FA-3 Similar to 1698 except 3 inch NEW (Odd Patterns) 700H Type 212 Vericon Camera Tube NEW TEST PATTERN 784 Schematic for Type 212 Vericon Camera 75.00 Printed on heavy cardboard Type 212 Vericon Deflection Yoke NEW Postpaid - Small #594 50¢ Type 212 Vericon Deflection Yoke and Focus coil-U Large #595 \$1.00 700J Type 5820 Orthicon Camera Tube-U 25.00 Stock #187 at \$5.95-Excellent Type 5820 Orthicon Deflection Yoke - Used

page 2

Type 5820 Orthicon Deflection Yoke NEW 210D1

Type 5820 Orthicon Focus Coil NEW

700LN

700IF

100.00 book on CCTV gives very comp-

100.00 rehensive course in TV cameras

and associated equipment.

FOR CLOSED-CIRCUIT APPLICATIONS VIA MONOSCOPE

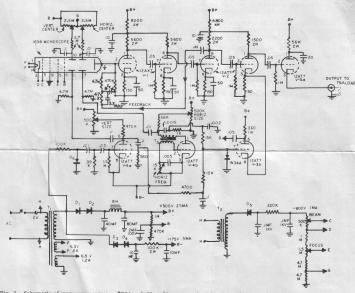


Fig. 1 - Schematic of monoscope camera. *Cf is 4 -40mmfd, compression trimmer. The sizes of the 47K and 3.9mmfd (in the feedback loop) can be altered if elimination of inser cannot be obtained within the range of Cf. variation individual virting practices frequently result in such out of range situations. However, careful witing using standard video amp practices should prevent this.

surveted on an 11 x 17 inch chastis. A photo showing the parts layout in our original unit is shown on the front cover. This arrangement proved to be quite adequate except that we would recommend anyone duplicating it to place the low voltage power transformer more to the left rear, since in the location shown its magnetic field more to the left rear, since in the location shown its magnetic field OPERATION; The part of the short of the same sufficiently signal tood resistor (470% grid test award time developed across the signal tood resistor (470% grid test award time as sufficiently amplified by a four stage video amplifier; the first as afficiently which incorporate negative feedback to offer the capacity force from the signal plate and signal lead to ground. The amplified signal is coupled to the 75 ohm line through the cathode follower, V3a, Sync-blanking pulses are mixed with the video in the cathole circuit of V2b. Note that the cathode of the 1698 is operated about 800 V above ground. Therefore the filament must also be operated above ground from a separate winding, Vertical sweep is obtained through a discharge stage, V4a locked to the AC line through a waveshaping and clipping network.

Horizontal sweep is obtained from a blocking oscillator, V4b, the combination sync-blanking pulse developed across the resistor in the discharge network of each deflection amp is nexed, clipped and inserted in the fourth video amp by the sync-blanking inserter, V3b, Focusing, beam current adjustment and centering controls are all conventional similar to those used in most scope circuits. The two power supplies are also quite straight-forward and should require no explanation... just one thing, it will be noticed that we have +300 and a -minus 175 instead of a single +475. The reason beling, 300 volts was

desited for the video amps and ync inserter but the additional voltage was advantageous for improved sweep linearity. Voltage, dropping resistors could have been used but we liked the fact that this allowed us to use readily available lower voltage capacitors both in the power supply and also in the coupling and sicharge networks. The method you choose will depend on your own personal perference.

TUME UP: Assuming no wiring errors or defective components, check out procedure is relatively simple compared to a flying spot or vidion. Bung an electrostatic type tube it's merely a matter of correctly setting the adjustment pots. Proceed in the following manner:

(1) Set all lumbs excent the heam (which should be as:

(1) Set all knobs except the beam (which should be set for maximum bias) to mid-range.

(2) Check to make sure monitor is properly adjusted on a local station prior to feeding video to it. (be sure it's properly terminated.)

(3) Now apply power and allow about 2 minutes for stabilization. The monitor should now be locked vertically since the vertical sweep is derived from the 60 CPS line. The horizontal soc is free running and unless you were lucky will probably nor be on frequency. If this is the case, adjust the frequency pot in the camera till the monitor is properly locked.

(4) You are now ready to see if you can get a pattern. Start variety the beam control (lowering the grid blas.) An image should insert a few parts of the start o

(5) The only thing remaining is to check the feedback in the video amplifiers. If you have either trailing whites or blacks following any of the areas on the pattern, feed back capacitor Cf is incorrectly set. Adjust it for minimum smear as observed on the monitor.

THAT's it you now have a fixed video pattern generator. See Fig. 2 for an off-the monitor picture of the 1698 pattern.

GENERAL .

Heater, for unipotential cathode

voltage current

direct interelectrode capacitances (approx) Grid No. 1 to all other electrodes. Signal electrode to all others

TENTATIVE DATA

R.C.A.

TYPE 1698

ONLY \$9,95

TWO INCH

MONOSCOPE

Focusing method Deflection

Target size Overall Length Maximum diameter Mounting position Cap

Base

Pin. 1 and 14 Heater 2 cathode

Pin grid no. 1 (beam) Pin internal connection, not used

Pin 5 grid no. 3 (focus) 6 grid no.

Pin Horz, deflection dj3 d.14

Maximum Ratings, Signal electrode, grids 1,3, & 4 Grid no. 2

negative bias value positive bias value

heater to cathode (peak) heater neg. with respect to cathode

heater pos. with respect to cathode Ambient temperature Typical operation

signal electrode grid no. 4 voltage

" for focus @ 0.2ua grid no. 4 current

grid no. 2 voltage

grid no. 1 voltage for visual cutoff with external shield

grid no. 2 current with 0.2ua current grid no. 4

Deflection factors (at Max grid no. 4 voltage) DJ1 and DJ2 DJ3 and DJ4

min. p.p. blanking voltage signal electrode current Resolution capability

Max. circuit values

Grid no. 1 circuit resistance

resistance in any deflecting electrode circuit 5.0 megs It is recommended that the deflecting electrode circuit resistance be approx. equal.

PARTS LIST D1, D2, D3, D4, D4. - Silicon diodes, 200ma, 400 PIV D5-HV diode, 1500W Barry Electronics
T-1 power xfmr, approx 300V at 50 ma, plus 2 fil windings as shown on diagram. T5-scope xfmr, 800V at 1 ma. T5-scope xfmr diagram 2 diagram 2 diagram 3 diagram 3 diagram 3 diagram 3 diagram 4 diagram 4 diagram 4 diagram 5 diagram 5 diagram 5 diagram 6 diag

> 6.3 ac or de 0.6 amp.

10 uuf 2.4 uuf Electrostatic Electrostatic

.72 diagonal 8 3/16"

SIMPLER than a flying spot scanner-LESS fussy than a Camera, this pattern generator produces a series of figures and numbers from the selfcontained pattern.

SIGNAL

PATTERN GENERATED

ELECTRODE

any DEFLECTION (ball)recessed small ANGLE Med. shell FOR THE VERT diheptal 14 pin & HORIZ PLATES Pin 9 grid no.2 IS 20 0 Pin 10 vert.defl.dj2

Pin 11 djl Pin 12 internal conn. Pin 13 Pin 14 heater Cap.signal electrode.

TARGET 1000 volts max. 20° 200 volts max. volts max. TOP OF GUN 140

10 volts max. 800 volts 850 volts 100 to 210 volts 800 volts

75 volts 75ua

50 to 68 vdc 38 to 52 vdc

30 volts Stock No. 700FA-2 ONLY \$9.95 plus postage - Ship. Wt. 3 lbs. 225 min.

Instructions Only - 50¢ - Stock No. 779 1.0 megs